


# EL323//EI324 Digital System Laboratory II

## LAB 3 : Design using VHDL

### Objective:

1. Can use the Quartus II and create the new project using VHDL
2. To know the assign pin of DE-0 in Quartus.
3. Design using VHDL
 
### LAB 3.1 (Altera Document: Laboratory Exercise 1, Part IV)



1. Create new Project name Lab3\_1.
2. Create new entity for 7-segment display in this below

$c_1 c_0$	Character
00	d
01	E
10	0
11	

Table 1. Character codes.

- Connect the  $c_1 c_0$  inputs to switches SW1 and SW0
- Connect the outputs of the decoder to the HEX0 display on the DE0 board. The segments in this display are called HEX00, HEX01, ..., HEX06, You should declare the 7-bit port

HEX0: OUT STD\_LOGIC\_VECTOR(0 TO 6);

3. Use the DE0 User Manual to define the DE0 pin.
4. Compile the code and program to DE0.

### Lab3.1 Code.

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

-- Simple module that connects the SW switches to the LEDG lights
ENTITY Lab3_1 IS
    PORT ( SW : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
          HEXO_D : OUT STD_LOGIC_VECTOR(6 DOWNTO 0) );
END Lab3_1;


ARCHITECTURE Behavior OF Lab3_1 IS
    SIGNAL s : STD_LOGIC_VECTOR (1 DOWNTO 0);
BEGIN
    s <= SW(1 DOWNTO 0);
    -- Recall that 7-Segments are active at LOW-level logic --
    -- character 'd' 0100001 SW 00
    -- character 'E' _____ SW 01
    -- character '0' _____ SW 10
    -- character '1' _____ SW 11
    --
    --      0
    --      ---
    --      | |
    --      5| |1
    --      |6 |
    --      ---
    --      | |
    --      4| |2
    --      | |
    --      ---
    --      3
    --
    -- the following equations describe display functions in (inverted)
    -- canonical SOP form

    HEXO_D(0) <= (s(1) AND s(0)) OR ((NOT s(1)) AND (NOT s(0)));
    HEXO_D(1) <= _____
    HEXO_D(2) <= _____
    HEXO_D(3) <= _____
    HEXO_D(4) <= _____
    HEXO_D(5) <= _____
    HEXO_D(6) <= _____

    ---- some additional VHDL code as necessary ----
END Behavior;
```



 **LAB 3.2 (Altera Document: Laboratory Exercise 1, Part V)**



1. Create new Project name Lab3\_2.
2. Create new entity for 7-segment display in this below

<i>SW<sub>9</sub></i>	<i>SW<sub>8</sub></i>	Character pattern		
00		d	E	0
01		E	0	d
10		0	d	E

**Table 2. Rotating the word DE0 on three displays**

- Connect the inputs switches Using SW<sub>9</sub> and SW<sub>8</sub> to select the display output
  - SW<sub>5-0</sub> is required to produce the patterns of characters as same as the Lab3\_1 and select to show like table 2.
3. Use the DE0 User Manual to define the DE0 pin.
  4. Compile the code and program to DE0.

### Lab3.2 Code.

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY Lab3_2 IS
    PORT ( SW : IN STD_LOGIC_VECTOR(9 DOWNT0 0);
          HEX0_D : OUT STD_LOGIC_VECTOR(6 DOWNT0 0);
          HEX1_D : OUT STD_LOGIC_VECTOR(6 DOWNT0 0);
          HEX2_D : OUT STD_LOGIC_VECTOR(6 DOWNT0 0);
          HEX3_D : OUT STD_LOGIC_VECTOR(6 DOWNT0 0);
          LEDG : OUT STD_LOGIC_VECTOR(9 DOWNT0 0));
END Lab3_2;
ARCHITECTURE Behavior OF Lab3_2 IS
    COMPONENT mux_2bit_3to1
        PORT ( S, U, V, W : IN STD_LOGIC_VECTOR(1 DOWNT0 0);
              M : OUT STD_LOGIC_VECTOR(1 DOWNT0 0));
    END COMPONENT;

    COMPONENT char_7seg
        PORT ( C : IN STD_LOGIC_VECTOR(1 DOWNT0 0);
              Display : OUT STD_LOGIC_VECTOR(6 DOWNT0 0));
    END COMPONENT;

    SIGNAL M_0, M_1, M_2, M_3 : STD_LOGIC_VECTOR(1 DOWNT0 0);
    SIGNAL Blank : STD_LOGIC_VECTOR(1 DOWNT0 0);

BEGIN
    LEDG(9 DOWNT0 8) <= SW(9 DOWNT0 8);
    Blank <= "11";
    -- first 7-segment --
    LEDG(3 DOWNT0 2) <= M_0;
    M3: mux_2bit_3to1 PORT MAP (SW(9 DOWNT0 8), SW(5 DOWNT0 4), SW(3 DOWNT0 2),
SW(1 DOWNT0 0), M_3);
    H3: char_7seg PORT MAP (M_3, HEX3_D);
    -- second 7-segment --
    M2: mux_2bit_3to1 PORT MAP (SW(9 DOWNT0 8), SW(3 DOWNT0 2), SW(1 DOWNT0 0),
SW(5 DOWNT0 4), M_2);
    H2: char_7seg PORT MAP (M_2, HEX2_D);
    -- third 7-segment --
    M1: mux_2bit_3to1 PORT MAP (SW(9 DOWNT0 8), SW(1 DOWNT0 0), SW(5 DOWNT0 4),
SW(3 DOWNT0 2), M_1);
    H1: char_7seg PORT MAP (M_1, HEX1_D);
    -- fourth 7-segment --
    H0: char_7seg PORT MAP (Blank, HEX0_D);
END Behavior;
```

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
-- implements a 2-bit wide 3-to-1 multiplexer
ENTITY mux_2bit_3to1 IS
    PORT ( S, U, V, W : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
          M : OUT STD_LOGIC_VECTOR(1 DOWNTO 0));
END mux_2bit_3to1;
ARCHITECTURE Behavior OF mux_2bit_3to1 IS
    SIGNAL m_0, m_1 : STD_LOGIC;
BEGIN
    m_0 <= _____
    M(0) <= _____ -- M(0)
    m_1 <= _____
    M(1) <= _____ -- M(1)
END Behavior;

LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY char_7seg IS
    PORT ( C : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
          Display : OUT STD_LOGIC_VECTOR(6 DOWNTO 0));
END char_7seg;
ARCHITECTURE Behavior OF char_7seg IS
    --
    -- 0
    -- ---
    -- | |
    -- 5| |1
    -- | 6 |
    -- ---
    -- | |
    -- 4| |2
    -- | |
    -- ---
    -- 3
    --

BEGIN
    Display(0) <= (NOT(C(1)) AND NOT(C(0))) OR (C(1) AND C(0));
    Display(1) <= _____
    Display(2) <= _____
    Display(3) <= _____
    Display(4) <= _____
    Display(5) <= _____
    Display(6) <= _____
END Behavior;

```

**Lab3.2 Answer Sheet**

The Mux 2bit 3 to 1 :

m\_0 <= \_\_\_\_\_

M(0) <= \_\_\_\_\_ -- M(0)

m\_1 <= \_\_\_\_\_

M(1) <= \_\_\_\_\_ -- M(1)

SW		Display 7 Segment	
SW1,3,5	SW0,2,4	Character	bits
0	0	'd'	_____
0	1	'E'	_____
1	0	'0'	_____
1	1	''	_____

Display(0) <= (NOT(C(1)) AND NOT(C(0))) OR (C(1) AND C(0));

Display(1) <= \_\_\_\_\_

Display(2) <= \_\_\_\_\_

Display(3) <= \_\_\_\_\_

Display(4) <= \_\_\_\_\_

Display(5) <= \_\_\_\_\_

Display(6) <= \_\_\_\_\_

SW										Display 7 Segment Character
SW9	SW8	SW7	SW6	SW5	SW4	SW3	SW2	SW1	SW0	
0	0	NC	NC	1	0	0	1	0	0	---
0	1	NC	NC	1	0	0	1	0	0	---
1	0	NC	NC	1	0	0	1	0	0	---
1	1	NC	NC	1	0	0	1	0	0	---
0	0	NC	NC	1	0	0	0	0	1	---
0	1	NC	NC	1	0	0	0	0	1	---
1	0	NC	NC	1	0	0	0	0	1	---
1	1	NC	NC	1	0	0	0	0	1	---
0	0	NC	NC	0	0	1	0	0	1	---
0	1	NC	NC	0	0	1	0	0	1	---
1	0	NC	NC	0	0	1	0	0	1	---
1	1	NC	NC	0	0	1	0	0	1	---
0	0	NC	NC	0	1	1	0	0	0	---
0	1	NC	NC	0	1	1	0	0	0	---
1	0	NC	NC	0	1	1	0	0	0	---
1	1	NC	NC	0	1	1	0	0	0	---

**Conclusion**

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

**Homework**

1. Follow the Lab3\_1 change character to this table. And Write the VHDL Code.

SW		Display 7 Segment	
SW1	SW0	Character	bits
0	0	'A'	-----
0	1	'3'	-----
1	0	'5'	-----
1	1	'C'	-----