

EL323//EI324 Digital System Laboratory II

LAB 5 : Conditional Statement

Objective:



1. Can use the Quartus II and create the new project using VHDL
2. To know the assign pin of DE-0 in Quartus.
3. Design using VHDL
4. To know conditional statement and adder with 7-segment

LAB 5.1 Full Adder


1. Create new Project name "adder".
2. Create new entity for adder in this below

c_i	x_i	y_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

(a) Truth table

  

(b) Karnaugh maps

 

(c) Circuit


```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;

ENTITY adder IS
    PORT ( Cin, X, Y: IN    STD_LOGIC ;
          S ,Cout : OUT   STD_LOGIC);
END adder ;


ARCHITECTURE Behavior OF adder IS
BEGIN
    S <= _____
    Cout <= _____
END Behavior ;

```

 

LAB 5.2 4bits ADDER using Full adder

 1. Create new Project name "adder4".
2. Create new entity for adder4 in this below



4-bits ADDER

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;

ENTITY adder4 IS
    PORT ( Cin      : IN   STD_LOGIC ;
          X, Y      : IN   STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          S         : OUT  STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          Cout      : OUT  STD_LOGIC ) ;
END adder4 ;

```

```

ARCHITECTURE Behavior OF adder4 IS
    COMPONENT adder
        PORT( X, Y, Cin : in STD_LOGIC;
              S, Cout : out STD_LOGIC);
    END COMPONENT;
    SIGNAL carry_sig : STD_LOGIC_VECTOR(3 DOWNTO 0) ;
BEGIN
    A1: adder port map (X(0), Y(0), Cin, S(0), carry_sig(0));
    A2: adder port map _____
    A3: adder port map _____
    A4: adder port map _____
END Behavior;

```

--////////////////////////////////////Full Adder////////////////////////////////////


```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;

ENTITY adder IS
    PORT ( Cin, X, Y: IN   STD_LOGIC ;
          S ,Cout : OUT  STD_LOGIC);
END adder ;





ARCHITECTURE Behavior OF adder IS
BEGIN
    S <= _____
    Cout <= _____
END Behavior ;

```

 

LAB 5.3 4bits ADDER using Full adder display with 7segment

1. Create new Project name "Lab5_3".
2. Create new entity for adder4 to display in 7 segment

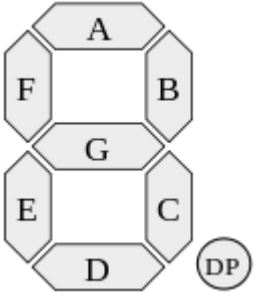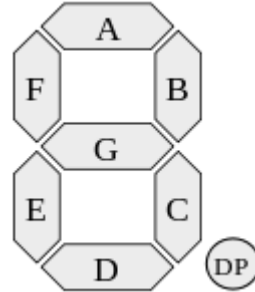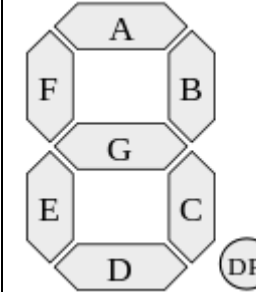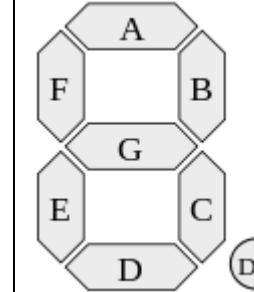Output	Hex3	Hex2	Hex1	Hex0
	X	Y dp <= (Cout)	Display Number	
7Segment				
Input	X (SW7-4)	Y (SW3-0)		

Cin (SW8)	X (SW7-4)	Y (SW3-0)	Hex1	Hex0
0	0	5	0	5
0	4	7	1	1
0	8	5	1	3
1	7	7	1	5
1	0	0	0	1

The Truth table of 4bit display 7 segment

3. SW7-4 as Input X , SW3-0 as Input Y , SW8 as Cin
4. Use the DE0 User Manual to define the DE0 pin.
5. Compile the code and program to DE0.

This pseudo-code can change the binary number to BCD that human known.

EX. 9 = 09, A = 10, B = 11, C = 12, D = 13, E = 14, F = 15

```

S = A + B + c0
If (S > 9) then
    Z0 = 10;
    P1 = 1;
Else
    Z0 = 0;
    P1 = 0;
End if
B0 = S - Z0
B1 = P1
    
```

LAB 5.3 Code

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;

ENTITY Lab5_3 IS
    PORT ( SW : IN STD_LOGIC_VECTOR(9 DOWNTO 0);
          LEDG : OUT STD_LOGIC_VECTOR(9 DOWNTO 0);
          HEX0 : OUT STD_LOGIC_VECTOR(6 DOWNTO 0);
          HEX1 : OUT STD_LOGIC_VECTOR(6 DOWNTO 0);
          HEX2 : OUT STD_LOGIC_VECTOR(7 DOWNTO 0);
          HEX3 : OUT STD_LOGIC_VECTOR(6 DOWNTO 0));

END Lab5_3 ;

ARCHITECTURE Behavior OF Lab5_3 IS
    COMPONENT adder
        PORT( X, Y, Cin : in STD_LOGIC;
              S, Cout : out STD_LOGIC);
    END COMPONENT;
    COMPONENT seg7display
        PORT(_____);
    END COMPONENT;

    SIGNAL Carry_Sig : STD_LOGIC_VECTOR(3 DOWNTO 0) ;
    SIGNAL Cin , Cout : STD_LOGIC ;
    SIGNAL X, Y : STD_LOGIC_VECTOR(3 DOWNTO 0) ;
    SIGNAL S,B0,B1,Z0,P1 : STD_LOGIC_VECTOR(3 DOWNTO 0) ;

BEGIN
    LEDG <= SW;
    X <= _____
    Y <= _____
    Cin <= _____
    HEX2(7) <= _____

    A1: adder port map (X(0), Y(0), Cin, S(0), Carry_Sig(0));
    A2: adder port map _____
    A3: adder port map _____
    A4: adder port map _____

    PROCESS(S)
    BEGIN
        IF (S > "1001") THEN
            Z0 <= _____
            P1 <= _____
        ELSE
            Z0 <= _____
            P1 <= _____
        END IF;
    END IF;
```

```
END PROCESS;
```

```
B0 <= _____
```

```
B1 <= _____
```

```
H1: seg7display port map (X,HEX2(6 DOWNT0 0));
```

```
H2: seg7display port map _____
```

```
H3: seg7display port map _____
```

```
H4: seg7display port map _____
```

```
END Behavior;
```

```
--////////////////////////////////////
```

```
-- FULL ADDER
```

```
LIBRARY ieee ;
```

```
USE ieee.std_logic_1164.all ;
```

```
USE ieee.std_logic_unsigned.all ;
```

```
ENTITY adder IS
```

```
    PORT ( Cin, X, Y: IN    STD_LOGIC ;
```

```
          S ,Cout : OUT  STD_LOGIC);
```

```
END adder ;
```

```
ARCHITECTURE Behavior OF adder IS
```

```
BEGIN
```

```
    S <= _____
```

```
    Cout <= _____
```

```
END Behavior ;
```

```
--////////////////////////////////////
```

```
-- 7 Segment Display
```

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.all;
```

```
ENTITY seg7display IS
```

```
    PORT(S : IN STD_LOGIC_VECTOR(3 DOWNT0 0);
```

```
          H : OUT STD_LOGIC_VECTOR(6 DOWNT0 0));
```

```
END seg7display;
```

```
ARCHITECTURE behavior OF seg7display IS
```

```
BEGIN
```

```
    PROCESS (S)
```

```
    BEGIN
```

```
    IF (S = "0000") THEN    H <= "1000000"; --0
```

```
    ELSIF (S = "0001") THEN H <= "1111001"; --1
```

```
    ELSIF (S = " ____ ") THEN H <= " _____ "; --2
```

```
    ELSIF (S = " ____ ") THEN H <= " _____ "; --3
```

```
    ELSIF (S = " ____ ") THEN H <= " _____ "; --4
```

```

ELSIF (S = "____") THEN H <= "_____"; --5
ELSIF (S = "____") THEN H <= "_____"; --6
ELSIF (S = "____") THEN H <= "_____"; --7
ELSIF (S = "____") THEN H <= "_____"; --8
ELSIF (S = "____") THEN H <= "_____"; --9
ELSE H <= "1111111";
END IF;
END PROCESS;
END behavior;

```

LAB5.3 Answer Sheet

Cin	Input X	Input Y	Cout	Hex 1	Hex0
0	0	1			
0	2	3			
0	4	5			
0	6	7			
0	8	9			
1	1	6			
1	2	7			
1	3	8			
1	4	9			
1	5	0			

Is this adder with 7segment has a limit? (If any limit, what is the limit of this lab? why? How we fix them?)

.....

.....

.....

.....

Conclusion

.....

.....

.....

.....

.....

.....