

EL323//EI324 Digital System Laboratory II


LAB 7 : Sequential Design and Hierarchy

Objective:


1. Can use the Quartus II and create the new project using VHDL
2. To know the assign pin of DE-0 in Quartus.
3. Design using VHDL
4. To know the counter and shift register

LAB 7.1 Counter

 1. Create new Project name "Counter4bit".
2. Create new entity for T Flip-flop in this below.



(a) Logic diagram

 

(b) Graphical symbol

Q	T	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

(c) Transition table

Clocked T flip-flop

 


Figure 1: A 4-bit counter.

3. The pushbutton KEY₀ as the Clock input, switches SW₁ and SW₀ as Enable and Reset inputs. The Hex₀ as the hexadecimal output.
4. Use the DE0 User Manual to define the DE0 pin.
5. Compile the code and program to DE0.

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity Counter4bit IS
    port(   enable, clk, rst : In std_logic;
          q, qbar : Inout std_logic_vector(3 DOWNTO 0);
          Hex, Out std_logic_vector(6 DOWNTO 0));
End Counter4bit;

Architecture Behavioral OF Counter4bit is
    Component TFF1 is
        Port(   t, rst, clk : In std_logic;
              q, qb : Out std_logic);
    End component;
    Component seg7display is
        PORT(S : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
             H : OUT STD_LOGIC_VECTOR(6 DOWNTO 0));
    End component;

    Signal k, l, m : std_logic;
    Begin
        k <= _____
        l <= _____
        m <= _____
        Counter1: _____
        Counter2: _____
        Counter3: _____
        Counter4: _____

        HEX1: _____

    End Behavioral;

```

```

Library IEEE;
Use IEEE.STD_LOGIC_1164.ALL;
Entity TFF1 IS
Port(  t,rst,clk : In std_logic;
      q,qb : Out std_logic);
End TFF1;


Architecture Behavioral OF TFF1 Is
Begin
    Process (clk,rst)
        Variable x : std_logic:='0';
        Begin
            If (clk' Event and clk=___) Then
                If ___ Then
                    x:=___;
                Elsif t=___ Then
                    x:=___;
                Else
                    x:=___;
                End if;
            End if;
            q<=x;
            qb<=not x;
        End Process;
    End Behavioral;

LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY seg7display IS
    PORT(S : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
         H : OUT STD_LOGIC_VECTOR(6 DOWNTO 0));
END seg7display;

ARCHITECTURE behavior OF seg7display IS
BEGIN
    -- // NEED CODE of Seg7display

END behavior;

```

 

Conclusion

.....

.....

.....


.....

.....

.....

LAB7.2 Counter Up/Down With load

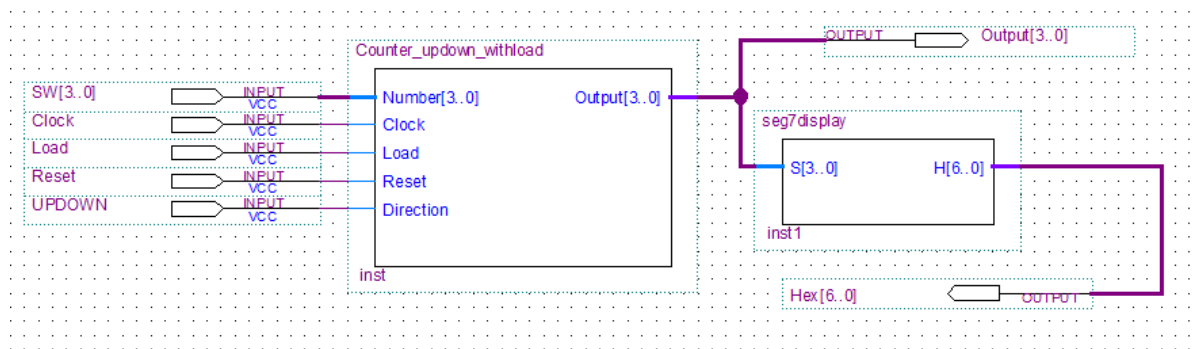1. Create new Project name "Counter_updown_withload".
2. Create new entity for counter in this below.



The Diagram of counter with load.

Input	Input FPGA
Number[3..0]	SW ₃ -SW ₀
Clock	Button ₂
UPDOWN(direction)	SW ₉
Load	SW ₈
Reset	SW ₇

Output	Output FPGA
Hex[6..0]	Hex1
Out[3..0]	LED ₃ -LED ₀

The input type	Description
Number	The input is start with this number
Load	The Load = 1 ,Load Number to start The Load = 0, Ready to UPDOWN.
Reset	The Reset = 0 , Clear the all bits The Reset = 1, Do nothing.
UPDOWN(direction)	The UPDOWN = 0 , number = number +1 The UPDOWN = 1 , number = number -1

3. Use the DE0 User Manual to define the DE0 pin.
4. Compile the code and program to DE0.

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;


entity Counter_updown_withload is
  port( Number: in std_logic_vector(3 downto 0);
        Clock: in std_logic;
        Load: in std_logic;
        Reset: in std_logic;
        Direction: in std_logic;
        Hex: out std_logic_vector(6 downto 0) );
        Output: out std_logic_vector(3 downto 0) );
end Counter_updown_withload;

architecture Behavioral of Counter_updown_withload is
  Component seg7display is
    PORT(S : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
          H : OUT STD_LOGIC_VECTOR(6 DOWNTO 0));
  End component;
  signal temp: std_logic_vector(3 downto 0);
begin
  process(Clock,Reset)
  begin
    if Reset='1' then
      temp <= _____;
    elsif ( Clock'event and Clock='1') then
      if Load='1' then
        temp <= _____;
      elsif (Load='0' and Direction='0') then
        temp <= _____;
      elsif (Load='0' and Direction='1') then
        temp <= _____;
      end if;
    end if;
  end process;
  Output <= _____
  HEX1: _____
end Behavioral;

LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY seg7display IS
  PORT(S : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        H : OUT STD_LOGIC_VECTOR(6 DOWNTO 0));
END seg7display;

ARCHITECTURE behavior OF seg7display IS
BEGIN
  -- // NEED CODE of Seg7display
END behavior;

```

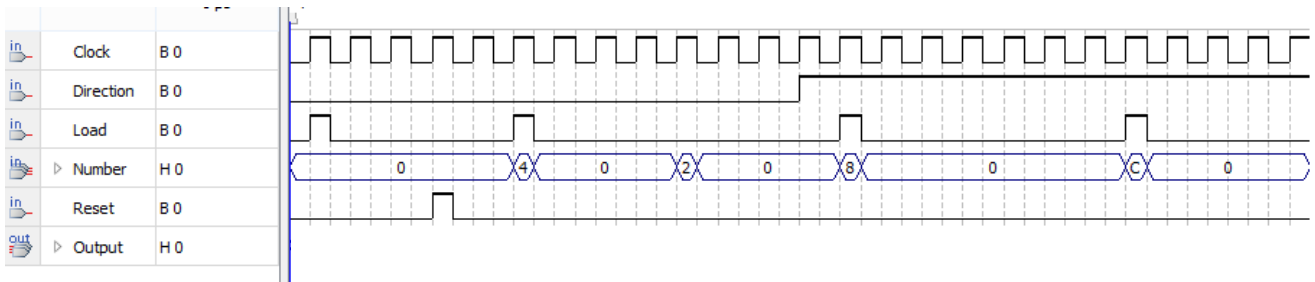

Number[3..0]	Clock	UPDOWN(direction)	Load	Reset	Out[3..0]	HEX
0 1 0 0	1 pulse	0	1	0		
0 0 0 0	2 pulse	0	0	0		
0 0 0 0	3 pulse	0	0	1		
0 0 0 0	1 pulse	1	0	0		
0 0 0 0	1 pulse	1	0	0		
1 0 0 0	1 pulse	1	1	0		
1 0 0 0	2 pulse	1	0	0		
1 0 0 0	3 pulse	1	0	0		

Conclusion

.....


.....

.....

.....

LAB7.3 Serial in and Serial out Shift Register

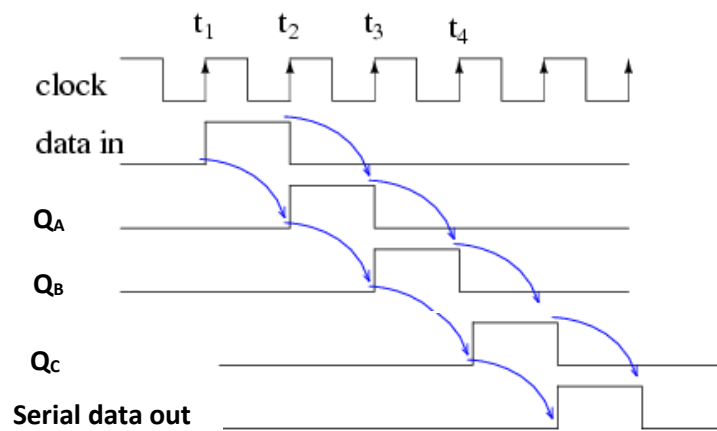
1. Create new Project name "Shift_register".
2. Create new entity for shift register in this below.



The time diagram of shift register 4 bit

LAB7.4 Parallel in- Parallel out Shift Register

 1. Create new Project name "Pin_Pout".
2. Create new entity for shift register in this below.



The diagram of Parallel in- Parallel out 4 bits.

```
Library IEEE;
Use IEEE.STD_LOGIC_1164.all;

Entity Pin_Pout is
  Port(
    din : in STD_LOGIC_VECTOR (3 downto 0);
    clk : in STD_LOGIC;
    reset : in STD_LOGIC;
    dout : out STD_LOGIC_VECTOR(3 downto 0)
  );
End Pin_Pout;

Architecture behavior of Pin_Pout is

Component D_Flip_Flop is
  PORT (
    Clk, D, Rst      : IN   STD_LOGIC;
    Q                : OUT  STD_LOGIC
  );
End Component D_Flip_Flop;

Begin

  u0 : D_Flip_Flop port map (clk,din(0),reset,dout(0));
  u1 : D_Flip_Flop port map (clk,din(1),reset,dout(1));
  u2 : D_Flip_Flop port map (clk,din(2),reset,dout(2));
  u3 : D_Flip_Flop port map (clk,din(3),reset,dout(3));

End behavior;

LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY D_Flip_Flop IS
  PORT ( Clk, D, Rst      : IN   STD_LOGIC;
         Q                : OUT  STD_LOGIC
  );
```




```

END D_Flip_Flop;

ARCHITECTURE Structural OF D_Flip_Flop IS
    SIGNAL Qa: STD_LOGIC;
BEGIN
    PROCESS (D, Clk, Rst)
    BEGIN
        IF (RST = '1') THEN
            Qa <= '0';
        ELSIF (Clk = '1' and Clk'event)
            Qa <= D;
        END IF;
    END PROCESS;
    Q <= Qa;
END Structural;

```

 

Conclusion

.....

.....

.....

.....